

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
B.Tech Degree S6 (S,FE) Examination December 2025 (2019 Scheme)

Course Code: ECT312
Course Name: DIGITAL SYSTEM DESIGN

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each question carries 3 marks.

Marks

- | | | |
|----|---|-----|
| 1 | List the State Assignment Rules for obtaining an optimal design. | (3) |
| 2 | Draw the state diagram to detect the overlapping Moore sequence 101. | (3) |
| 3 | Differentiate a primitive flow table from an ordinary flow table. | (3) |
| 4 | What is a race in asynchronous sequential circuits? Briefly explain the two types of races. | (3) |
| 5 | Write a short note on Jitter. | (3) |
| 6 | Explain Dynamic Hazards with an e.g. | (3) |
| 7 | What is the principle of Path sensitization method and mention its advantages. | (3) |
| 8 | List the 3 restrictions imposed on networks for applying the Kohavi's Algorithm. | (3) |
| 9 | What are the advantages of FPGA? | (3) |
| 10 | Write a note on Programmable Interconnects. | (3) |

PART B


Answer one full question from each module, each question carries 14 marks.

Module I

- | | | |
|----|--|-----|
| 11 | a) Design a clocked synchronous Serial Binary Adder using Moore model using D flip-flop for realization. | (8) |
| | b) Analyse the general components of an ASM block with the aid of well labelled diagrams. | (6) |

OR


- | | | |
|----|---|-----|
| 12 | a) Analyse the following CSSN and derive the next state and output equations. Obtain the excitation table, transition table, state table and state diagram. | (8) |
|----|---|-----|

 

 - b) Obtain a minimal state table for a clocked synchronous sequential network having a single input line 'x' in which the symbols 0 and 1 are applied and a single output line 'z'. An output of 1 is to be produced if and only if the 3 input symbols following two consecutive input 0's consist of at least one 1. An example of input/output sequences that satisfy the conditions of the network specifications is:
- x= 0100010010010010000000011
z= 00000010000001000000000001

Module II

- 13 a) Analyse the asynchronous sequential network given below by forming the excitation/transition table, state table, flow table and flow diagram. The network operates in the fundamental mode with the restriction that only one input variable can change at a time.



- b) Explain in detail the design of an ALU.

OR

- 14 a) Design a fundamental mode asynchronous sequential circuit with two inputs x_1 and x_2 and with one output z . Whenever x_2 is '1' input x_1 is transferred to z . When x_2 is '0' the output data does not change for any change in x_1 . (9)
- b) Explain any one race free state assignment method in asynchronous sequential network with example. (5)

Module III

- 15 a) Examine the possibility of hazard in the AND- OR logic circuit whose Boolean function is given by $f(x_1, x_2, x_3) = \pi(0, 1, 2, 6)$. Show that there is a static 0 hazard when x_1 and x_2 are equal to 0 and x_3 goes from 0 to 1. Draw the hazard free circuit. (8)
- b) Describe the operation of mixed operating mode (MOM) asynchronous sequential circuit with the aid of standard model. (6)

OR

- 16 a) Draw the logic diagram of the POS expression $Y = (x_1 + x_2')(x_2 + x_3)$. Show that there is a static-0 hazard when x_1 and x_3 are equal to 0 and x_2 goes from 0 to 1. Find a way to remove the hazard by adding one or more gates (8)
- b) Explain clock skew? Differentiate between positive and negative clock skew. (6)


Module IV

- 17 a) What is a fault? How are faults classified? Define the terms: fault detection, fault location, test vector, Essential test vector, selective test vector and minimal complete test set. Explain the steps involved in the testing process. (8)
- b) Draw the logic diagram for the expression $f = (x_1x_2 + x_3')(x_3 + x_4)$. Find the test vectors for detecting the faults at input line, x_3 using Boolean difference method. (6)

OR

- 18 a) For the circuit given in figure below, find the test vectors for the following faults using path sensitization method. (7)

 (i) SA0 at x_3 (ii) SA1 at x_3 (iii) SA0 at g (iv) SA1 at g .



- b) Find the test vectors for all SA0 and SA1 faults in the circuit whose Boolean function is $f = x_1x_2 + x_2'x_3 + x_3x_4$ using Kohavi's algorithm. (7)

Module V

- 19 a) Explain the architecture of XC 4000 FPGA family. (7)
 b) With suitable sketches, describe the internal structure of XC4000 Configurable Logic Block (CLB). (7)

OR

- 20 Draw and explain the features of architecture of Xilinx 9500 CPLD family. Also explain the function block, input-output block and switch matrix architecture. (14)
