

Reg No :

Name :

**MAR ATHANASIUS COLLEGE OF ENGINEERING, KOTHAMANGALAM**

(Govt. Aided Autonomous Institution)

Third Semester B.Tech. Degree (SAY) Examination, February, 2026

Course Code: B24EC2T03


Course Name: NETWORK THEORY

Max. Marks: 100


Duration:3 Hours

PART - A: 30 Marks (10 Qns x 3 Marks)**Answer all questions**

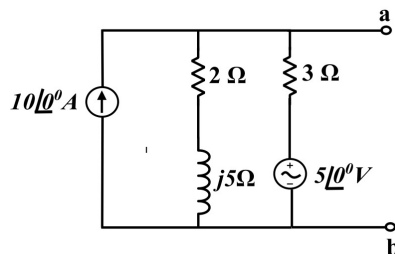1. A series RLC circuit consists of a $10\ \Omega$ resistor and a 60 mH inductor. If the circuit operates at 25 Hz with a power factor leading by 45° , determine the frequency at which the circuit will be in resonance.
2. A network contains a current source common to two meshes. How is this handled in mesh analysis?
3. For the maximum power transfer, find the value of Z_L in the network shown for the following cases:
 - a) Z_L is variable resistance
 - b) Z_L is complex impedance, with variable resistance and variable reactance,
 - c) Z_L is complex impedance with variable resistance and fixed reactance of $j5\Omega$.



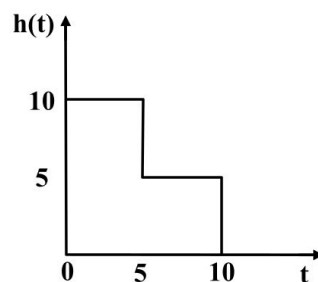4. Superposition theorem is not applicable to networks containing nonlinear elements. Why?
5. Find the Laplace transform of the function $h(t)$ shown in figure.




6. Derive the expression for the current in a series RC circuit when the input is a unit step signal of amplitude V?
7. Determine the time-domain response of the circuit when the pole lie on the left half of s-plane and right half of s-plane.
8. Obtain the pole-zero plot of the function. $F(s) = \frac{s(s+2)}{(s+1+j1)(s+1-j1)}$.
9. Draw the equivalent circuit of a two port network in terms of h-parameters.
10. The h-parameter of a two port network is given as, $h_{11}=25$, $h_{12}=0.2$, $h_{21}=2$, $h_{22}=0.04$. Check whether the given network is symmetric?

PART - B: 70 Marks (5 Qns x 14 Marks)

Answer any One full question from each module.


Module 1

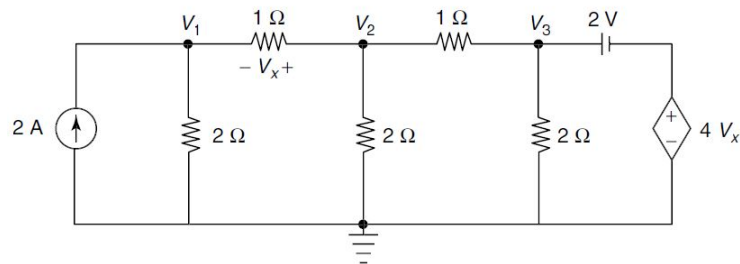11. Analyze the network to set up the node voltage equations and solve for V_1 , V_2 and V_3 .




OR

12. Analyze the network to derive the equations needed to find V_y in the network shown.

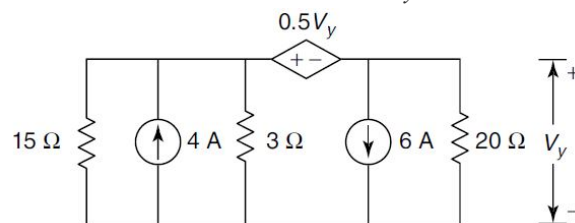


Module 2

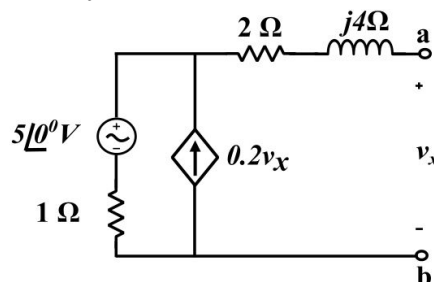13. Analyze the given network and determine the Thevenin equivalent across terminals $a - b$. Discuss how the equivalent circuit simplifies the analysis of connected loads.



OR

14. Evaluate the given circuit using Norton's theorem to determine I_0 .

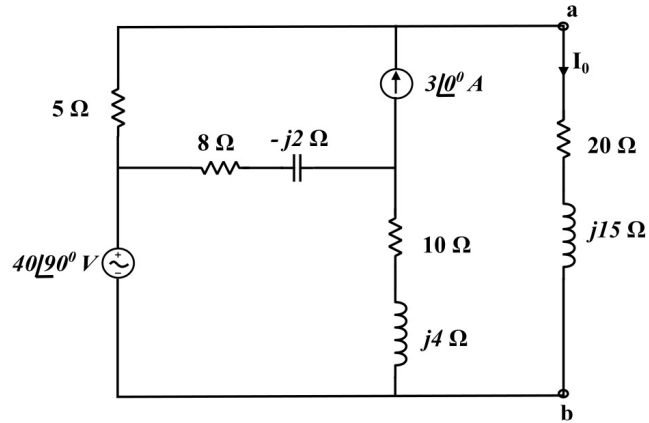


Module 3

15. Find the inverse Laplace transform of the transformed function

$$F(s) = (s^2 - 15s - 11)/((s + 1)(s - 2)^2)$$


OR

16. In the network shown, the switch is closed at $t = 0$, the steady-state being reached before $t = 0$. Determine current through inductor of 3H.

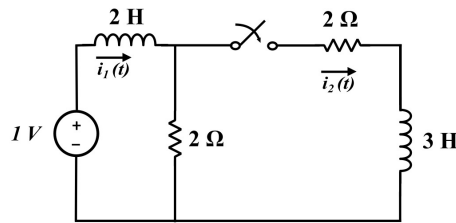


Module 4

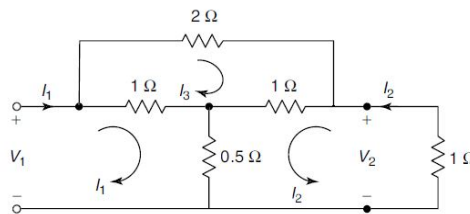17. For the resistive bridged T network shown, find V_2/V_1 , V_2/I_1 , I_2/V_1 and I_2/I_1 .




OR

18. For the network shown, find the driving-point admittance Y_{11} and transfer admittance Y_{12} .

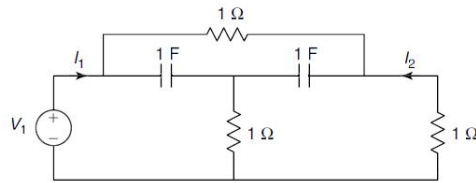


Module 5

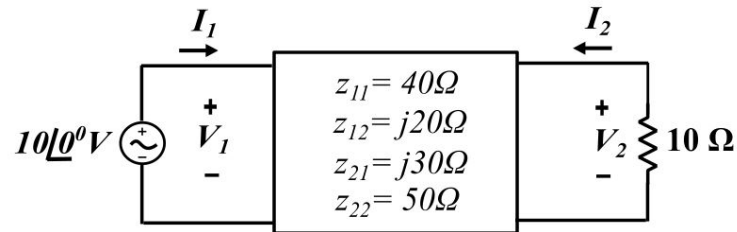19. a) Find I_1 and I_2 in the circuit shown. (4 marks)



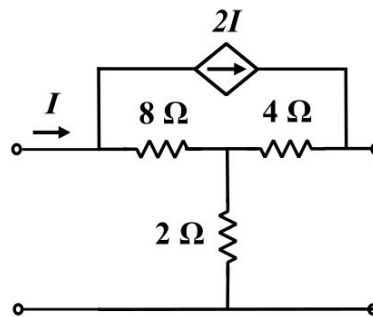- b) Determine the Y parameters for the two-port shown. (10 marks)



OR

20. Analyze the two-port network to derive its Y-parameters.

